
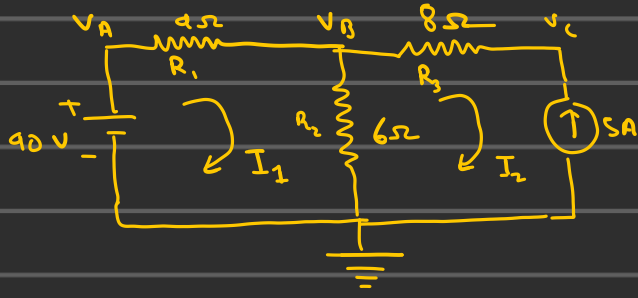


# Mesh Current Problems

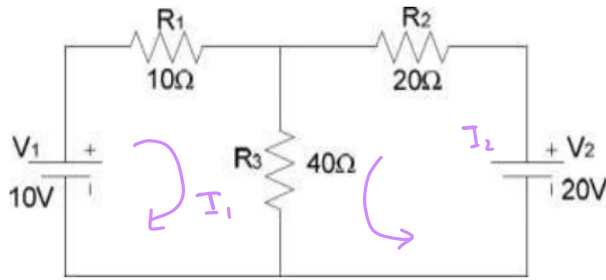

from -ve to +ve  $V \uparrow +v$   
+ve to -ve  $V \downarrow -v$

**Example:** Find the current flow through each resistor using **mesh analysis** for the circuit below.



**Solution:**

So the equations would be :- Ⓜ So the logic

$$I_1 R_1 + I_1 R_3 + I_2 R_3 = V_1$$

$$\& I_2 R_2 + I_2 R_3 + R_3 I_1 = V_2$$

$$I_1 10 + I_1 40 + I_2 40 = 10$$

$$\& I_2 20 + I_2 40 + I_1 40 = 20$$

$$\text{So } I_1 + 40 I_2 = 10$$

$$\& 60 I_2 + 40 I_1 = 20$$

upon solving both of the equation simultaneously.

$$50 I_1 + 40 I_2 = 10$$

$$5 I_1 + 4 I_2 = 1 \times 4 = 20 I_1 + 16 I_2 = 4$$

$$40 I_1 + 60 I_2 = 20$$

$$- 4 I_1 + 6 I_2 = 2 \times 5$$


$$\begin{array}{r} 20 I_1 + 16 I_2 = 4 \\ -20 I_1 - 30 I_2 = 10 \\ \hline 14 I_2 = 6 \end{array}$$

$$14 I_2 = 6$$

$$\boxed{I_1 = -0.143 \text{ A}}$$

$$\boxed{I_2 = 9/14}$$

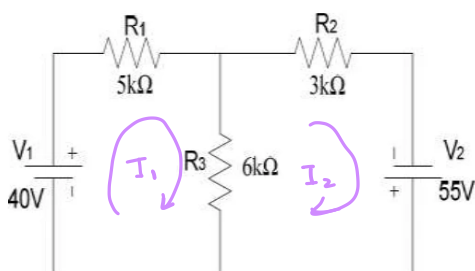**Example:** Find the current flow through each resistor using mesh analysis for the circuit.



Take  
current in  
clock wise  
direction  
preferably

$$I_1 R_1 + I_1 R_3 - I_2 R_3 = V_1$$

$$I_1 5 + I_1 (6) - I_2 (6) = 40$$

$$11 I_1 - I_2 6 = 40$$

$$\Delta I_2 R_2 + I_2 R_3 - I_1 R_3 = V_2$$

$$\Delta I_2 (3) + I_2 6 - I_1 6 = 55$$

$$\Delta 4 I_2 - I_1 6 = 55$$


$$11 I_1 - 6 I_2 = 40 \times 6 \Rightarrow 66 I_1 - 36 I_2 = 240$$

$$-6 I_1 + 4 I_2 = 55 \times 11 \Rightarrow \underline{-66 I_1 + 44 I_2 = 605}$$

$$8 I_2 = 845$$

In this we've to find in mA so you'd need to divide by 1k upon that you'd get the answer  $I_1 = 10.95 \text{ mA}$  &  $I_2 = 13.41 \text{ mA}$ .

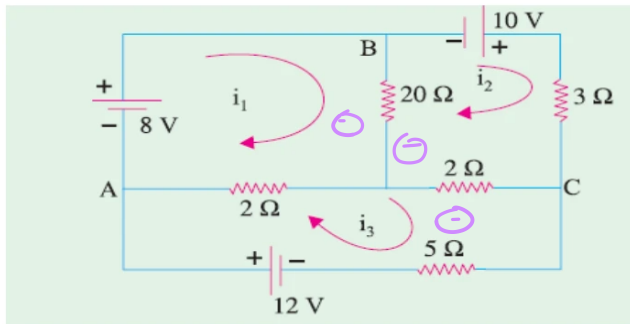**Example:** Determine the current in the  $5\Omega$  resistor using Mesh Analysis.



$$8 + (i_1 - I_2)20 + (I_1 - I_3)2 = 0 \quad \text{for mesh ①} \quad I_1 = x$$

$$10 + (I_2 - I_1)20 + (I_2 - I_3)2 = 0 \quad \text{for mesh ②} \quad I_2 = y$$

$$12 + (I_3 - I_1)2 + (I_3 - I_2)2 + I_3 5 = 0 \quad \text{for mesh ③} \quad I_3 = z$$

$$8 + 20 I_1 - 20 I_2 + 2 I_1 - 2 I_3 = 0$$


$$8 + 22 I_1 - 20 I_2 = 0$$

$$10 + 10 I_2 - 20 I_1 + 2 I_2 - 2 I_3 = 0 \Rightarrow 10 + 12 I_2 - 20 I_1 = 0$$

$$12 + 2 I_3 - 2 I_1 + 2 I_3 - 2 I_2 + I_3 5 \Rightarrow 12 + 9 I_3 - 2 I_1 - 2 I_2 = 0$$

$$I_3 = 6.33 \text{ A}$$


**Nodal Analysis :-**

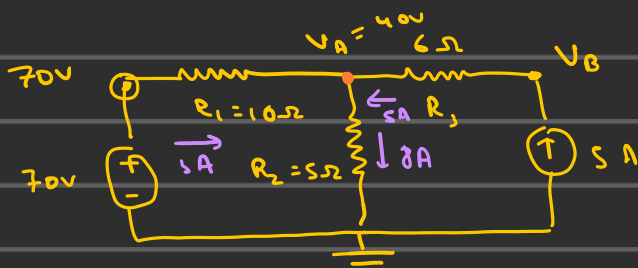

• → node

electropotential at GND = 0V

to find  $V_A$  &  $V_B$

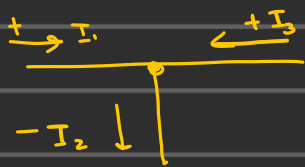

towards junction  $\rightarrow$  +ve, away -ve

$$V = IR$$

$$\frac{V}{R} = I$$

$$I_1 - I_2 + I_3 = 0$$

$$I = \frac{V_H - V_L}{R} = \frac{70 - V_A}{10} = I_1 \quad \text{high} \rightarrow \text{low electro potential.}$$

$$\frac{70 - V_A}{10} - \frac{V_A}{5} + 5 = 0 \Rightarrow 70 - V_A - 2V_A + 50 = 0$$

$$70 - 3V_A + 50 = 0$$

$$= 120 = 3V_A \quad \boxed{V_A = 40}$$

$$I_1 = \frac{V_1}{R_1} = \frac{30V}{10\Omega} = 3A \quad I_2 = \frac{V_2}{R_2} = \frac{40}{5\Omega} = 8A$$



$$V = IR \quad V_3 = I_3 R_3$$

$$V_H - V_L = I_3 R_3$$

$$V_B - V_A = I_3 R_3$$

$$V_B - 40 = 30$$


$$\boxed{V_B = 70V}$$

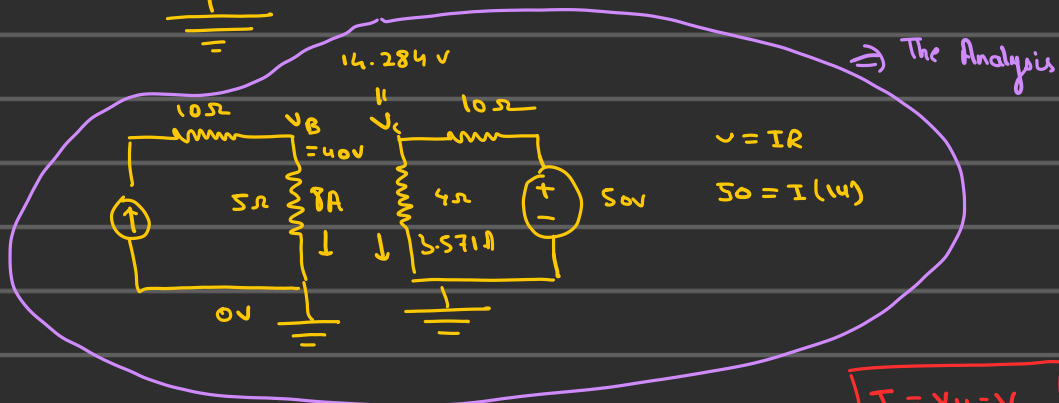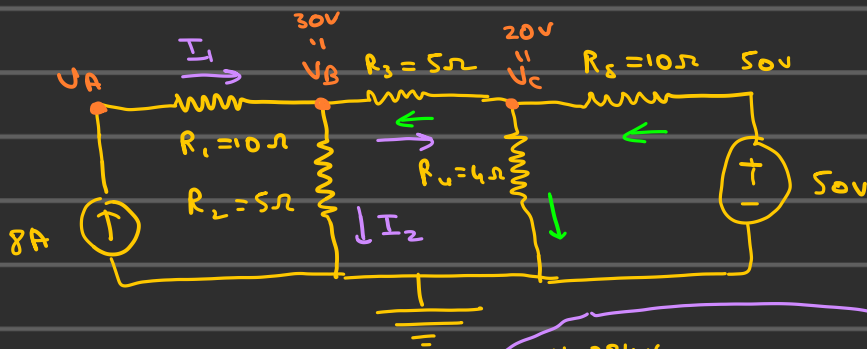

$$V = IR$$

$$50 = I(14)$$

$$\boxed{I = \frac{V_H - V_L}{R}}$$

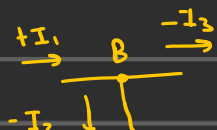

$$I_1 - I_2 - I_3 = 0$$

$$\left( 8A - \frac{(V_B)}{5} - \frac{(V_B - V_C)}{5} = 0 \right)$$

$$I_3 = \frac{V_B - V_C}{R_3}$$

$$40 - V_B - V_B - V_C = 0$$

$$40 - 2V_B - V_C = 0$$

$$\boxed{-2V_B + V_C = -40}$$

$$\begin{aligned} -4V_B + 2V_C &= -80 \\ + \quad 4V_B - 11V_C &= -100 \\ \hline -9V_C &= -180 \end{aligned}$$

$$\boxed{V_C = 20} *$$

$$-2V_B + 20 = -40$$

$$-2V_B = -60$$

$$\boxed{V_B = 30} *$$

for node C:-

$$I_2 - I_4 + I_5 = 0$$

$$\frac{V_B - V_C}{5} - \left(\frac{V_C}{4}\right) + \frac{50 - V_C}{10} = 0$$

$$4V_B - V_C - 5V_C + 100 - 2V_C = 0$$

$$4V_B - 11V_C + 100 = 0$$

$$V = IR$$

$$V_A - 30 = I \cdot R_1$$

$$V_A - 30 = 8(10)$$

$$\boxed{V_A = 110V}$$

$$I_2 = \frac{V_A - V_C}{R} = \frac{30 - 0}{5} = \underline{\underline{6A}}$$

$$I_4 = \frac{20 - 0}{4} = 5A$$


$$I_3 = \frac{V_A - V_C}{R_3} = \frac{30 - 20}{5} = 2A$$

$$I_5 = \frac{50 - 20}{10} = \underline{\underline{3A}}$$

watch nodal, superposition, Thevenin, nodal, maximum power transfer.

9 min      11 min      15 min

## Superposition Theorem

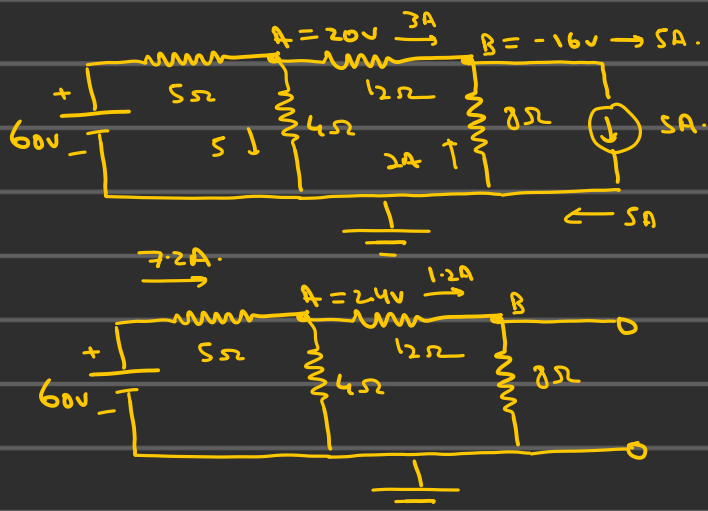

$$V_A = -7R$$

$$20 || 4 = \left( \frac{1}{20} + \frac{1}{4} \right)^{-1} = \left( \frac{1}{20} + \frac{5}{20} \right)^{-1}$$

$$= \left( \frac{6}{20} \right)^{-1} = \frac{20}{6} = \frac{10}{3}$$

$$\boxed{R_T = 8.33\Omega}$$


$$I = \frac{V}{R_T} = \frac{60}{8.333} =$$

$$I_{4A} = \frac{V}{R} = \frac{24}{4} = \underline{\underline{6A}}$$

$$V_A = 60V - 7.2(5) = 24V$$


$$V_B - V_A = -IR$$
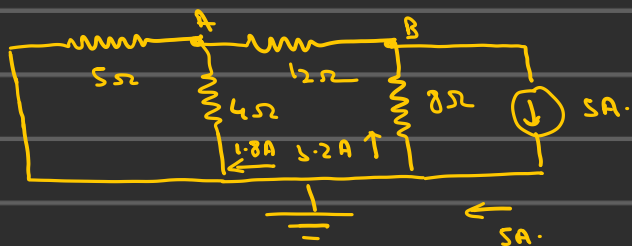
$$V_D = 24 - 1.2(14) \quad V_A = 24V ; V_B = 9.6V ; I_4 = 6A.$$



$$[5 \parallel 12] \parallel 8$$
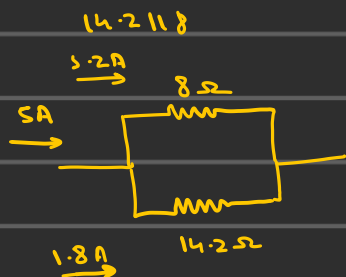
$$= \left( \frac{1}{5} + \frac{1}{12} \right)^{-1} \parallel 8 = 2.22 \parallel 8 = 14.2$$



$$5A \cdot \frac{14.2}{22.2} = 3.2A$$




$$1.8 \left( \frac{5}{9} \right) = 1A$$

$$V_B = -8(3.2) = -25.6V ; V_A = -4V, V_D = -25.6V \quad I_4 = 1A$$

Now upon applying superposition.  $I = \frac{V}{k} = \frac{40V}{5} = 20 - 3(12) = -16$

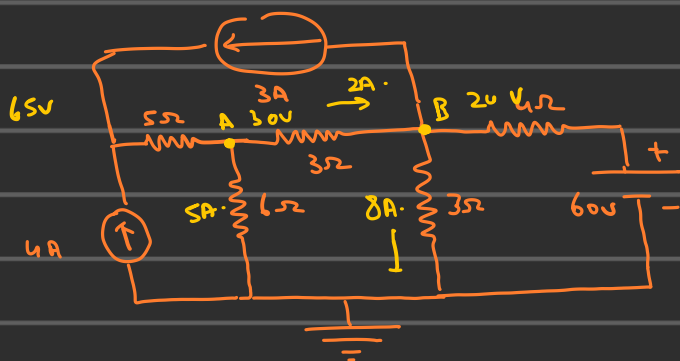
Solve circuit with one power at a time & then add.




$$V_B = 5.84V$$

$$V_A = 10.56V$$

$$R_T = 4.7143\Omega$$

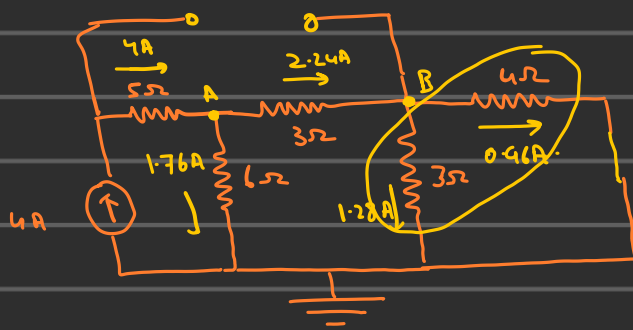

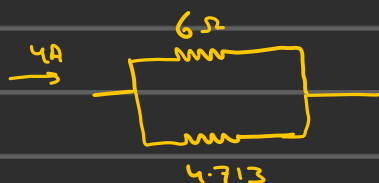
$$3 \parallel 4 = \left( \frac{1}{3} + \frac{1}{4} \right)^{-1} + 3 = 4.7143\Omega$$




$$4A \cdot \frac{4.7143}{10.7143}$$

$$2.24A \cdot \frac{4}{7} = 1.28A$$

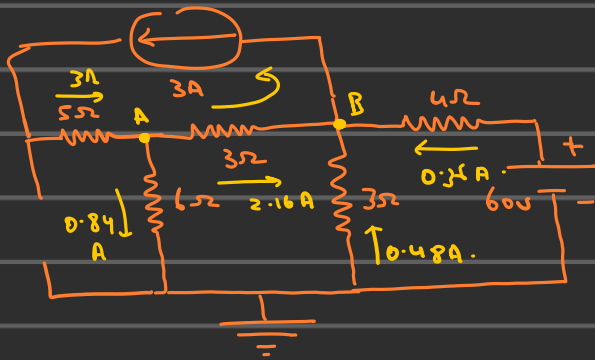

$$V_a = 0.84(6) = 5.14 \text{ V}$$
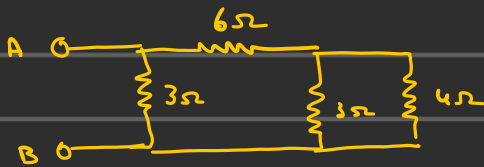
$$V_D = 5.64 - 2.16A(3.52) = -1.44 \text{ V}$$




$$3 \parallel 4 + 6 = \left( \frac{1}{3} + \frac{1}{4} \right)^{-1} + 6 = 7.7143 \Omega$$

(current divider circuit)



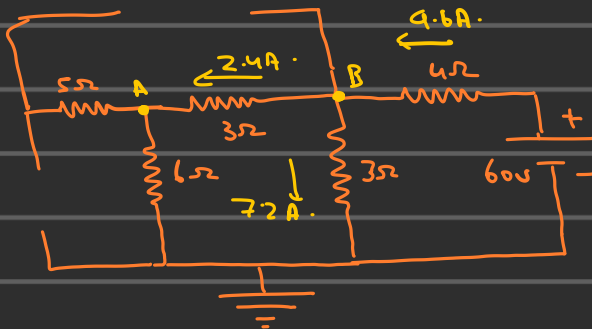
$$3A \cdot \frac{7.7143}{10.7143} = 2.16A$$



$$9 \parallel 4 = \left( \frac{1}{9} + \frac{1}{4} \right)^{-1} + 4 = 6.25 \Omega$$
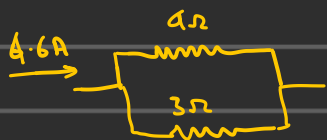
$$I = \frac{V}{R_T} = \frac{60 \text{ V}}{6.25 \Omega}$$




$$9.6A \cdot \frac{9 \Omega}{12 \Omega}$$

$$V_B = 60 - 9(9.6) = 21.6 \text{ V}$$

$$V_A = V_B - I_R = 21.6 - 2.4A(3)$$

$$V_A = 14.4, \quad V_B = 21.6$$

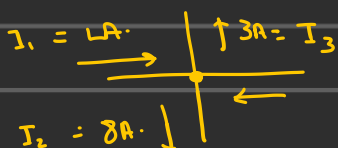$\therefore$  the final  $V_A = 30 \text{ V}$  &  $V_B = 24 \text{ V}$



$$I_1 + I_2 + I_3 + I_4 = 0$$




$$2 + (-8) + (-3) + I_4 = 0$$

$$-6 - 3 + I_4 = 0$$

$$\therefore \boxed{I_4 = 9 \text{ A}}$$

$$I = V/R = \frac{60 - 24}{4} = \frac{36}{4} = 9 \text{ A}$$

# Thevenin's Theorem

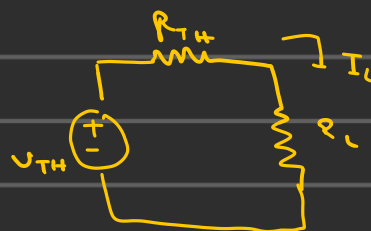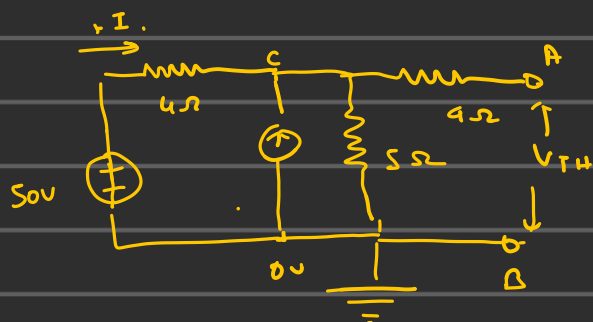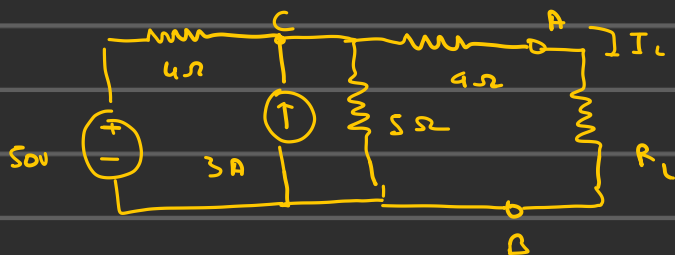

$$\left(\frac{1}{4} + \frac{1}{5}\right)^{-1} + 4 = 11.2 \Omega$$

To calculate thevenin voltage

$$V_L = V_A = V_{TH}$$

$$I_1 + I_2 - I_3 = 0 \quad I = V/R$$


$$\left(\frac{50 - V_L}{4} + 3 - \frac{V_L - 0}{5} = 0\right) 20$$

$$250 - 5V_L + 60 - 4V_L = 0$$

$$5(50 - V_L) + 60 - 4V_L = 0$$

$$\frac{310}{9} = \frac{4V_L}{9}$$

$$V_L = 34.4 \text{ V}$$

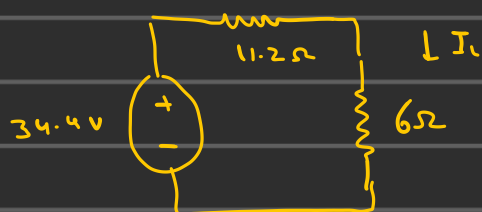


$$I_L = \frac{V}{R_T}$$

$$= \frac{34.4}{11.2 + 6}$$

$$= \frac{34.4}{17.2}$$

$$= \underline{\underline{2A}}$$

A	B	C	F
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	0

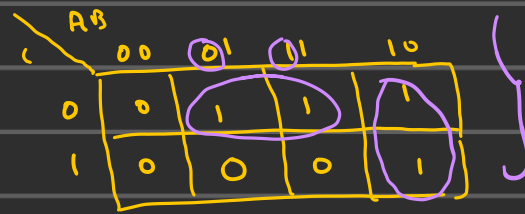

This is a Kmap.

Can circle 1, 2, 4, 8 1's

$$F = B\bar{C} + A\bar{B}$$

$$= 1(\bar{1}) + 0(\bar{1})$$

$$= 1(0) + 0(0)$$

$$= 0 + 0 = 0$$

→ to find what variables don't change.